

Hardware hack for the tea light upgrade

Lunartec 6er-Set Akku-LED-Teelichter mit Ladestation, Fernbedienung, 15 Std.



Hardware Instructions




On the following 11 pages I explain how you can replace the existing chip of a rechargeable tea light with a standard ATiny85 microcontroller on which you can install your own firmware.

Firmware can be found here:


<https://github.com/tscha70/LEDCandle>



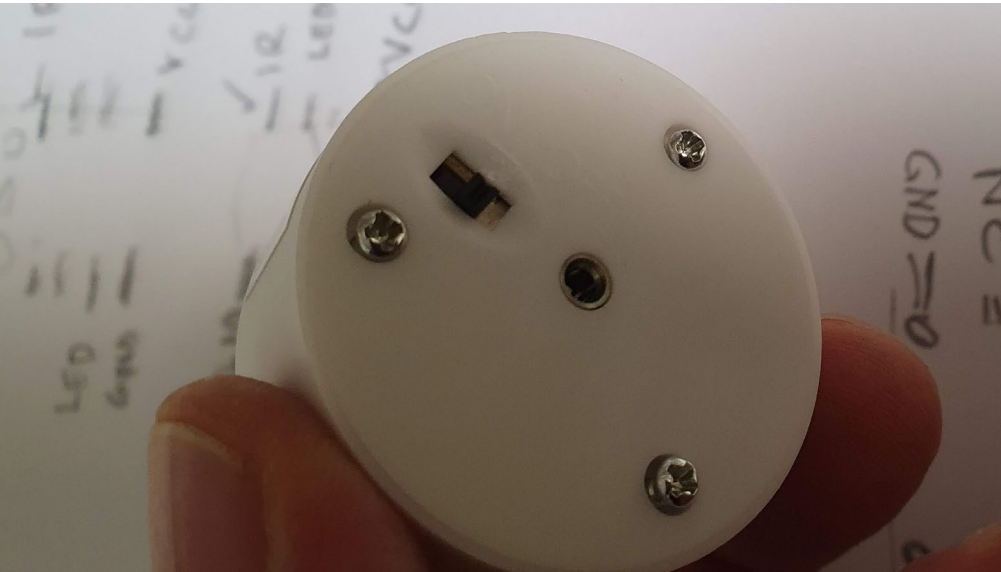
Open the candle by removing the screws on the base plate. And remove the base plate.




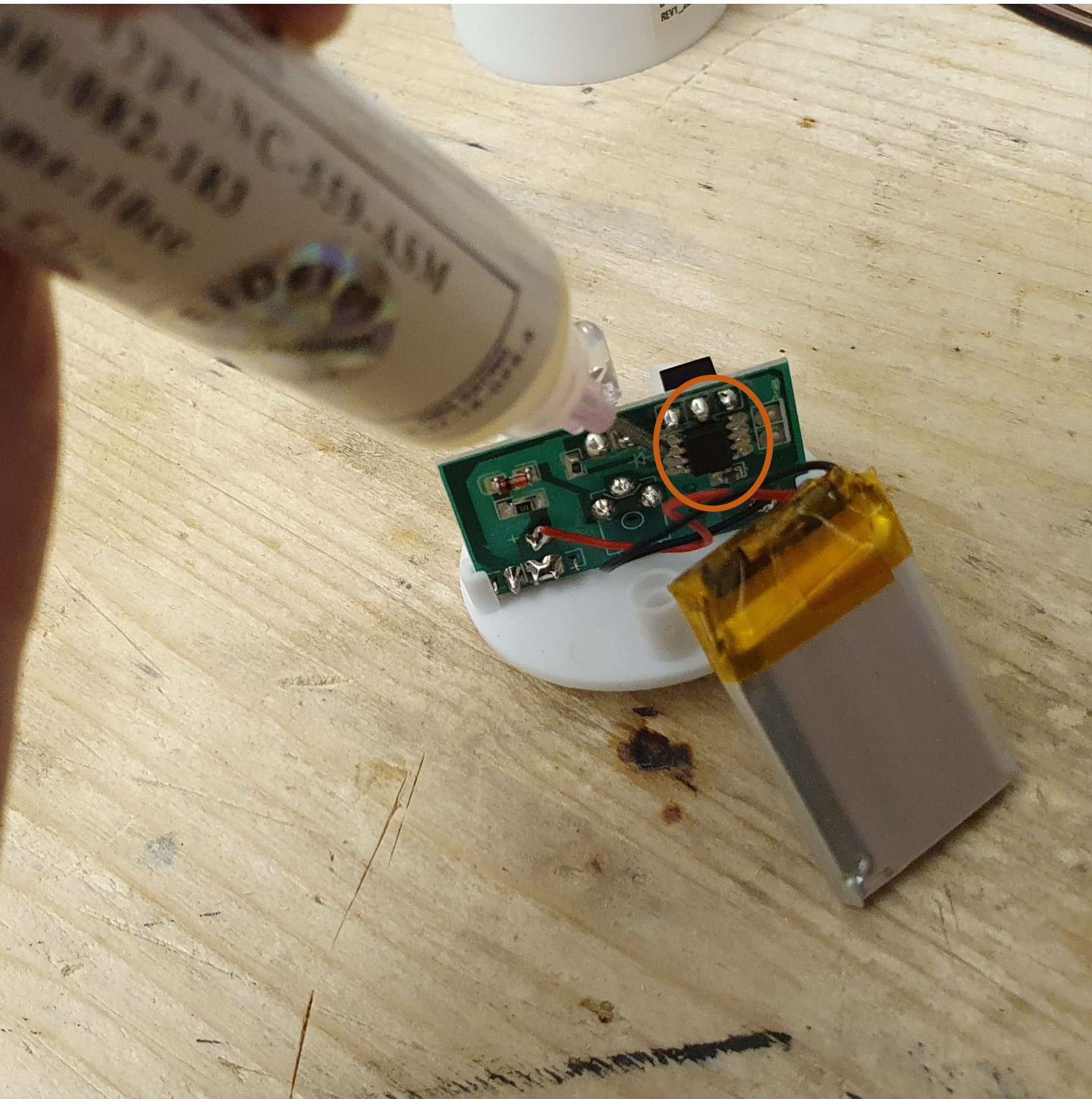
Desolder the chip by first applying flux and then using a hot soldering iron.



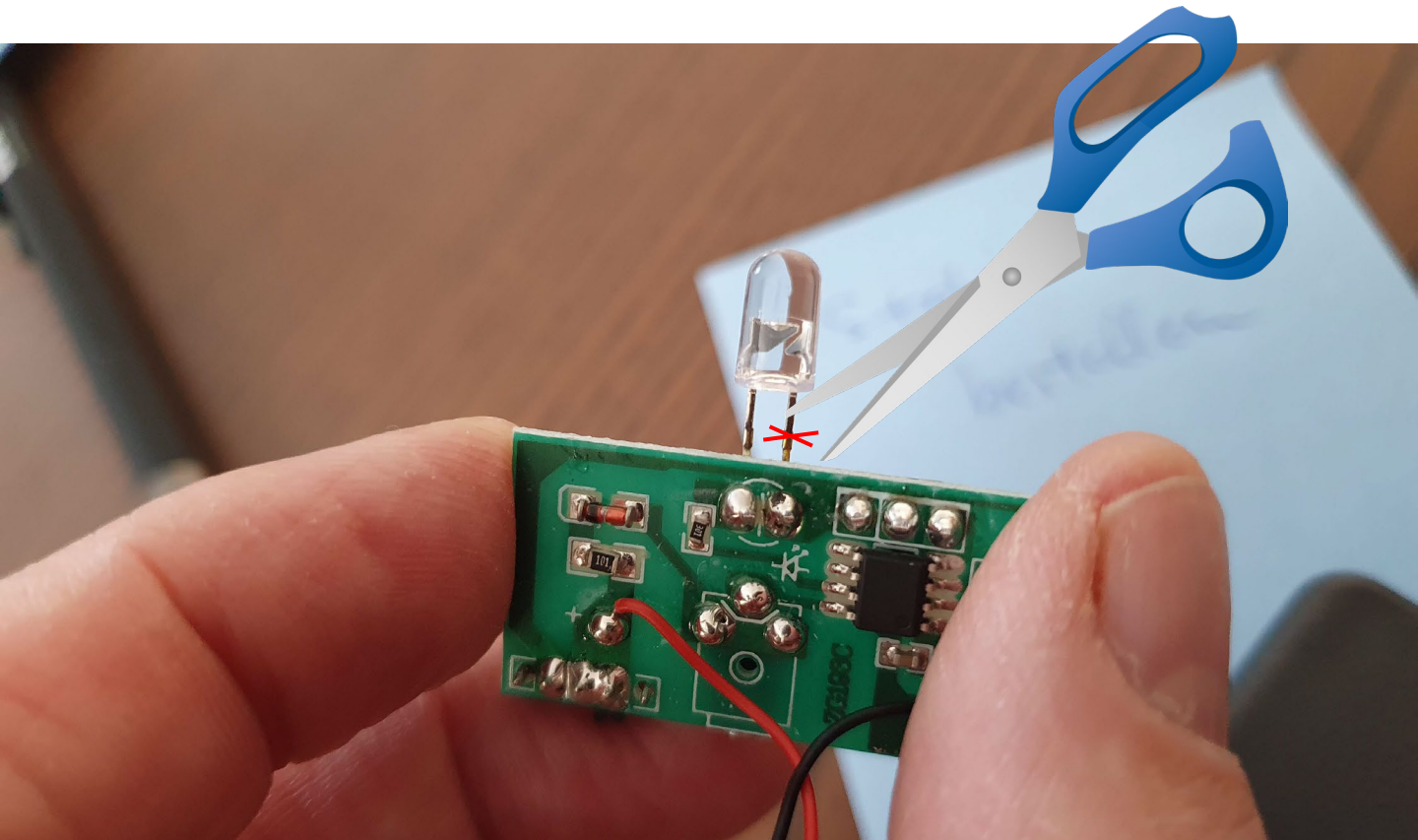Separate the right leg of the LED from the circuit board.



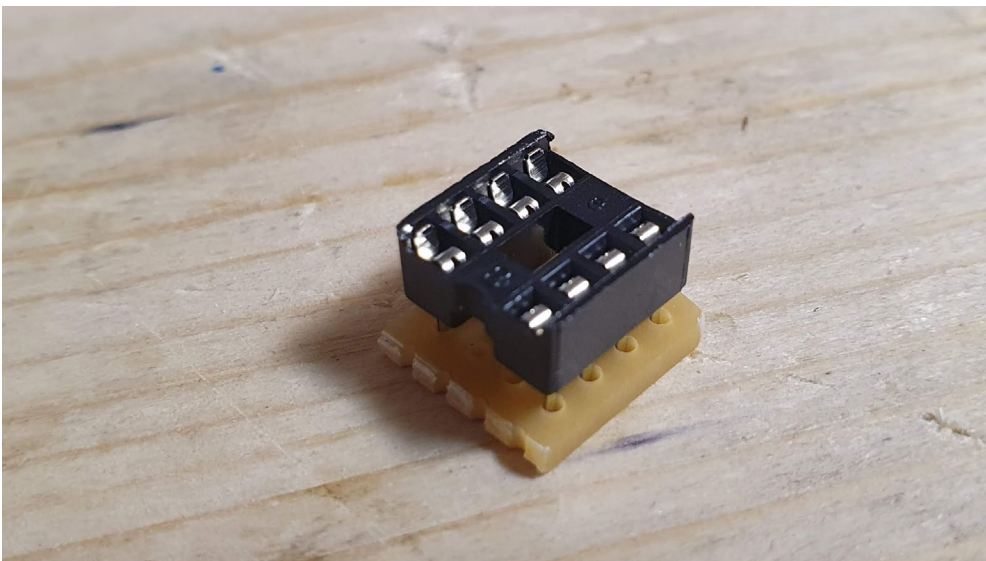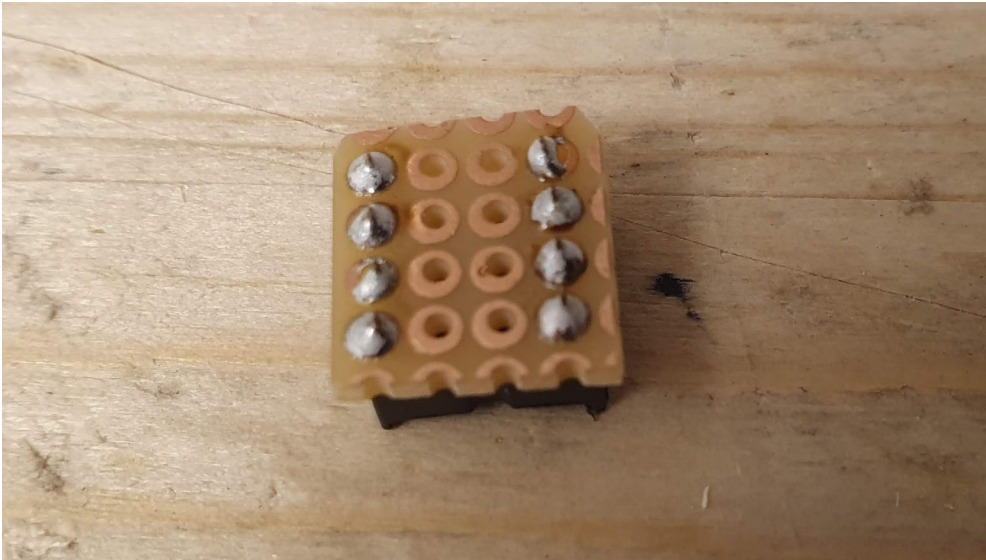
Prepare an 8-DIP IC socket on a piece of perfboard.



Solder Step 1 of 4

```
//          +-\\/-+
// (5) PB5  1|      |8  Vcc
// (3) PB3  2|      |7  PB2
// (4) PB4  3|      |6  PB1 (1) LED output (PWM)
//          GND  4|      |5  PB0 (0) IR Input
//          +-----+
```

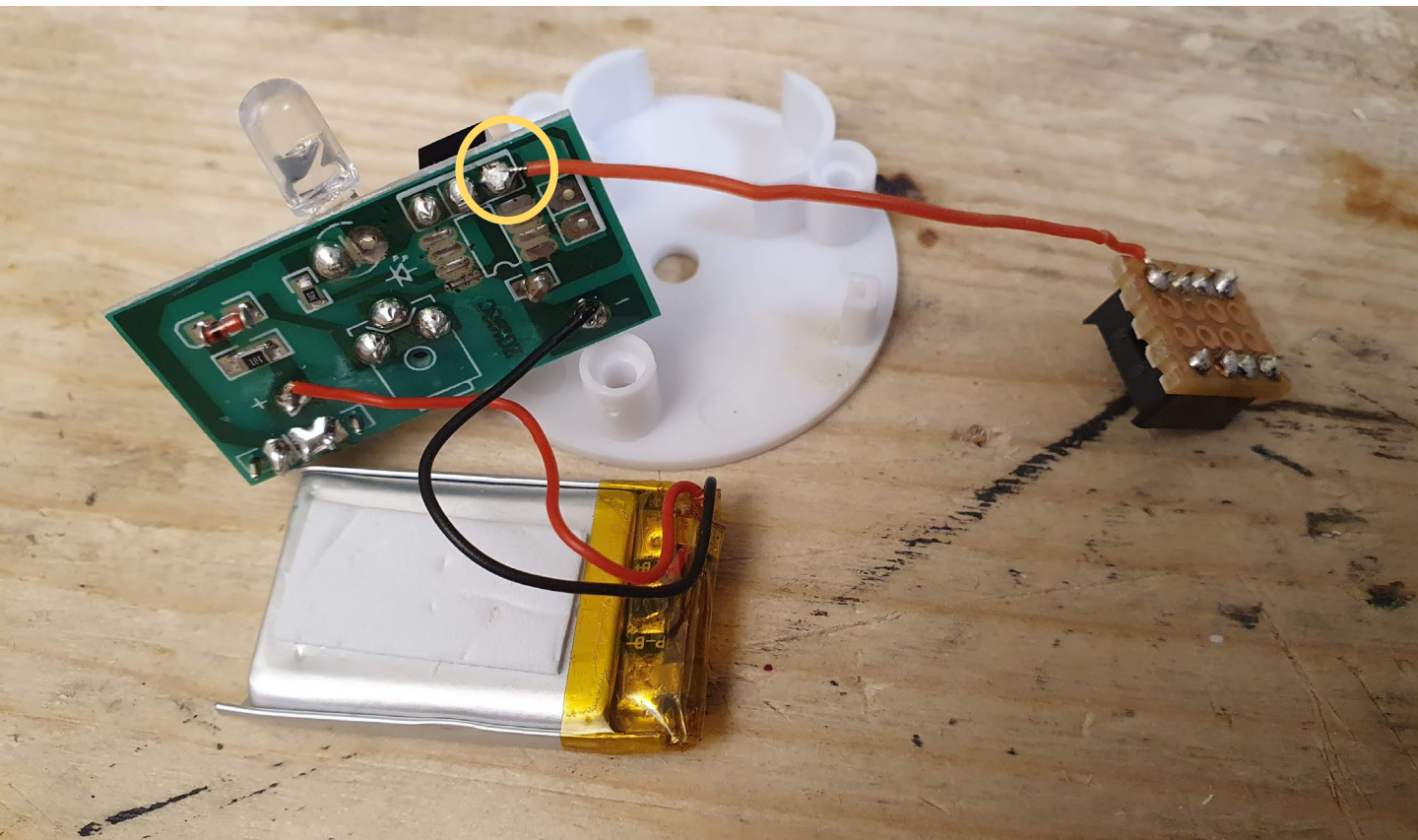
The IR-Connection is soldered to pin 5 (PB0) on the socket.



Solder Step 2 of 4

```
//          +-\/-+
// (5) PB5  1|      |8  Vcc
// (3) PB3  2|      |7  PB2
// (4) PB4  3|      |6  PB1 (1) LED output (PWM)
//          GND 4|      |5  PB0 (0) IR Input
//          +-----+
```

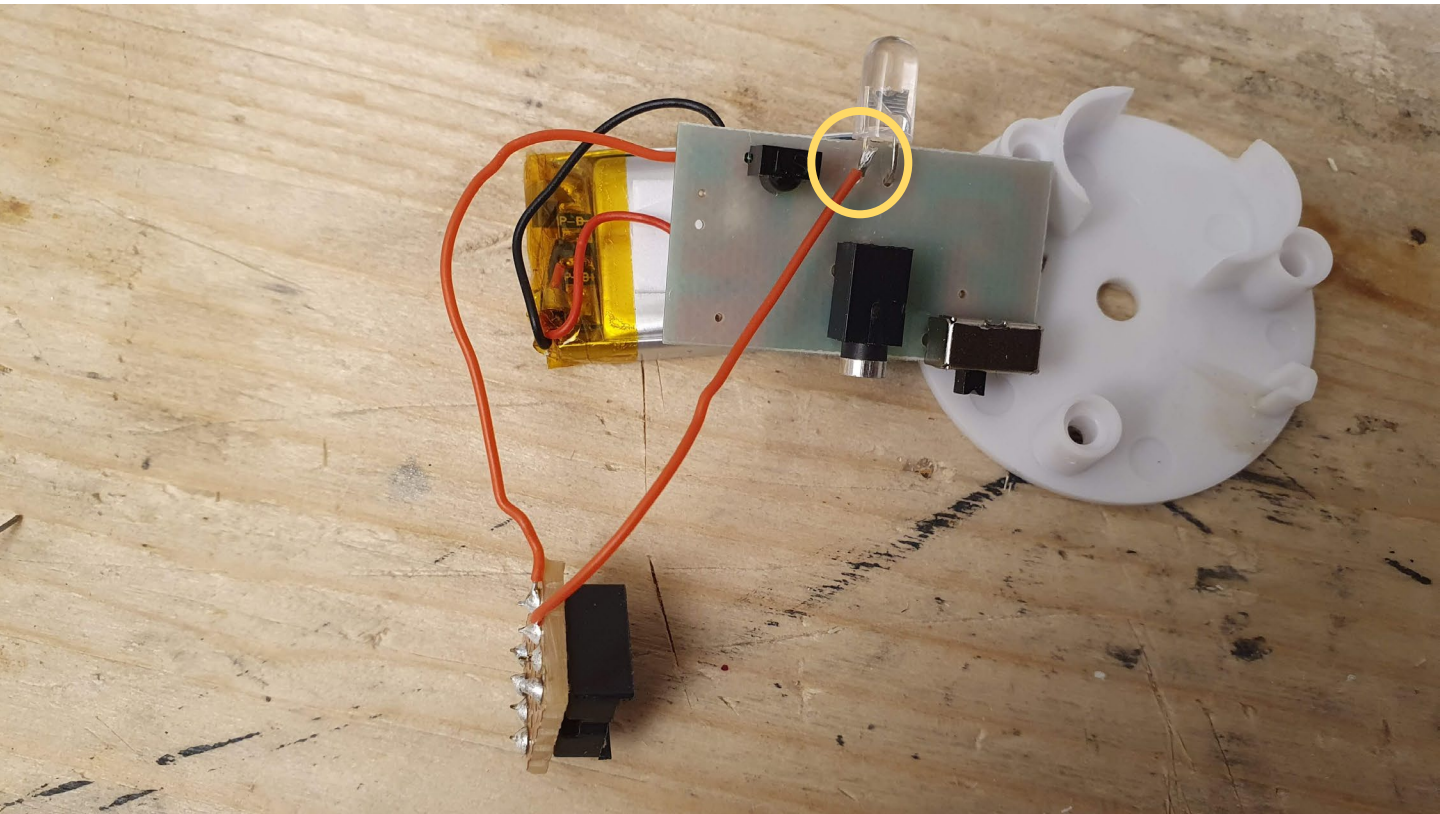
The positive LED-pin is soldered to pin 6 (PB1) on the socket.
(Remember, the LED-leg is disconnected from the circuit board)



Solder Step 3 of 4

```
//          +-\/-+
// (5) PB5  1 |      | 8  Vcc
// (3) PB3  2 |      | 7  PB2
// (4) PB4  3 |      | 6  PB1 (1) LED output (PWM)
//          GND 4 |      | 5  PB0 (0) IR Input
//          +-----+
```

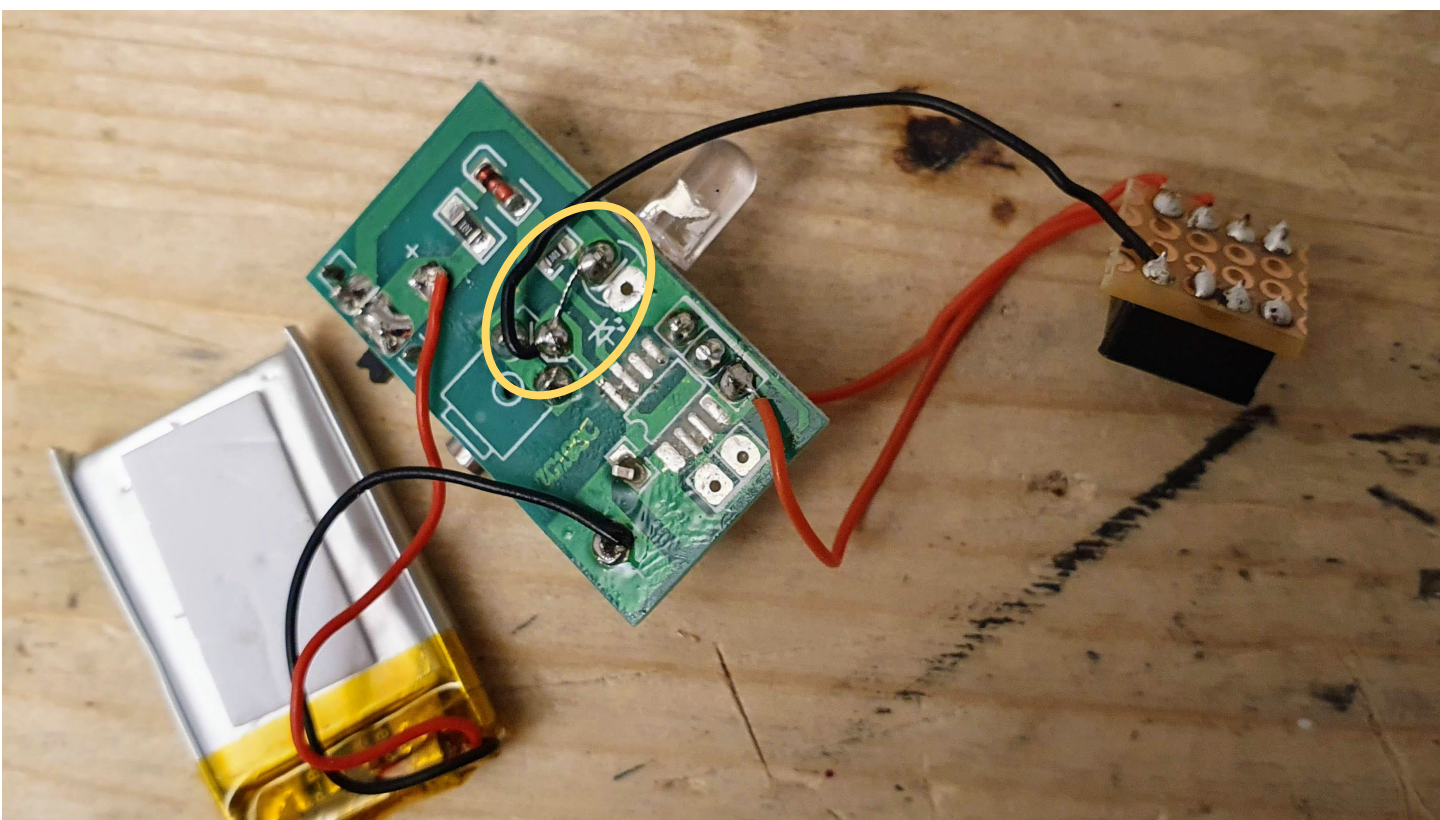
The ground pin 4 is soldered to the circuit board. The two points in the picture below must also be connected at the same time. This means that the LED is earthed.




Solder Step 4 of 4

```
//          +-\/-+
// (5) PB5  1|      |8  Vcc
// (3) PB3  2|      |7  PB2
// (4) PB4  3|      |6  PB1 (1) LED output (PWM)
//          GND 4|      |5  PB0 (0) IR Input
//          +-----+
```

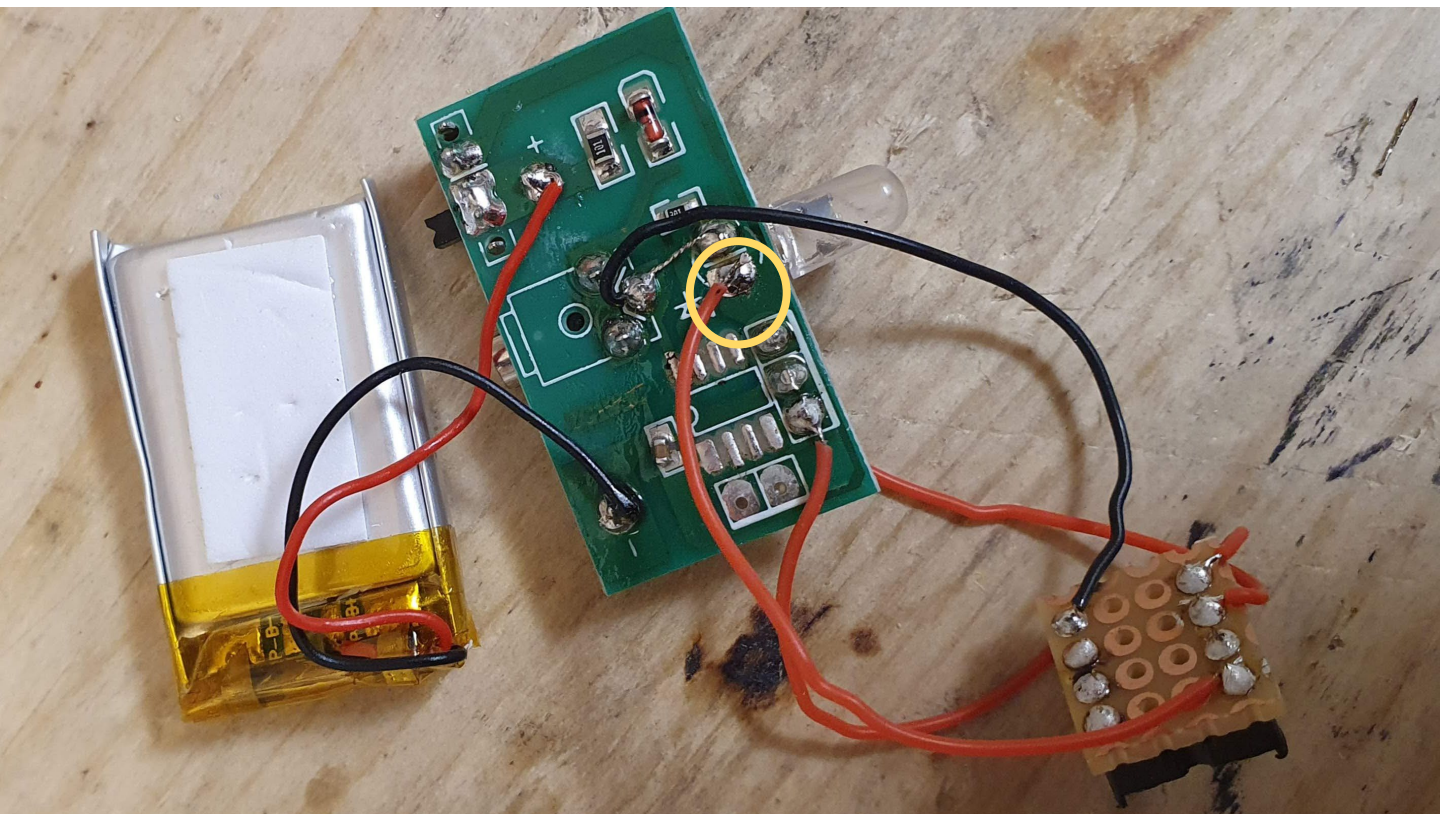
In the last step, the positive power source (VCC) is connected to pin 8 of the socket.



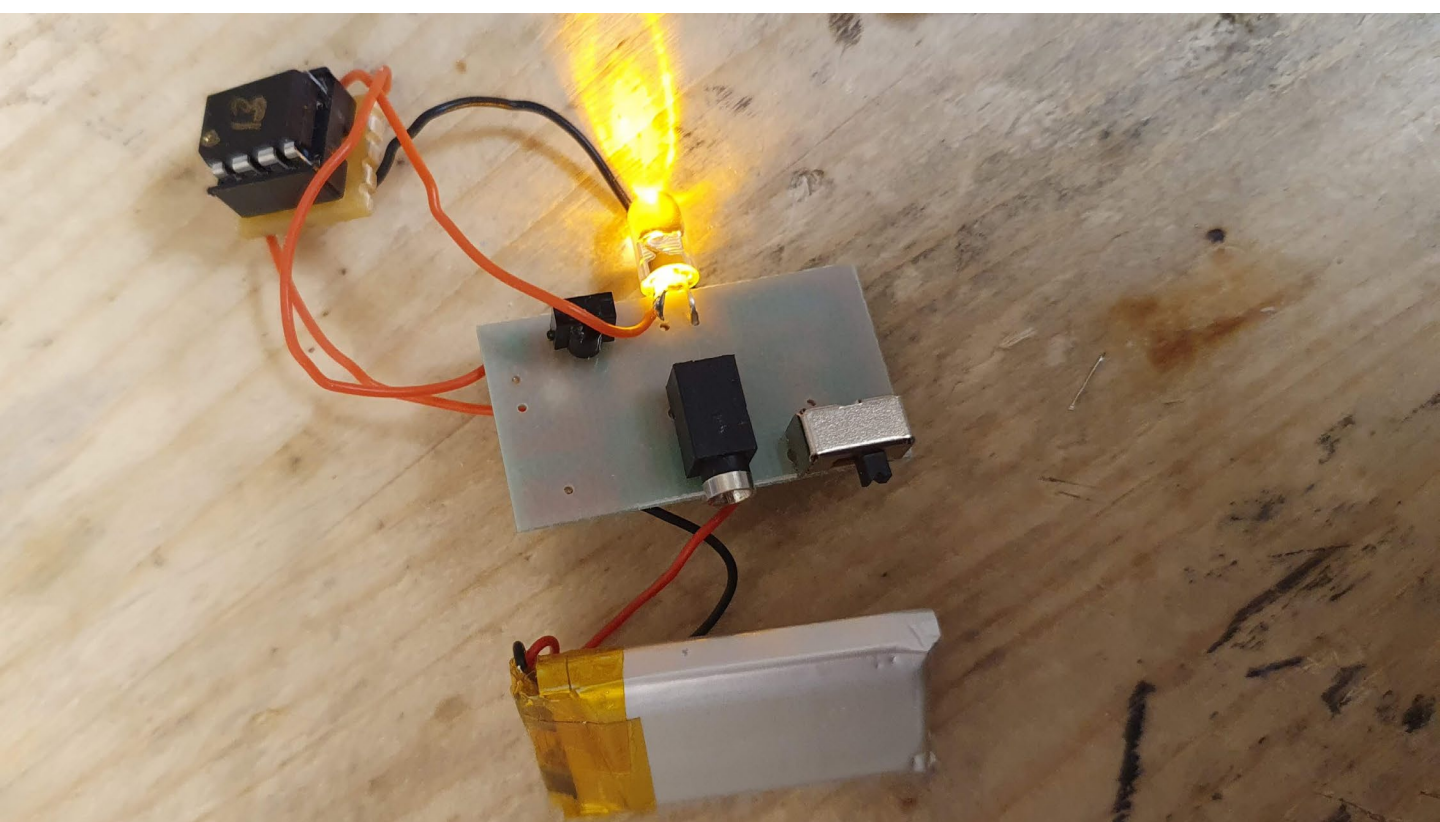Now you can insert your own microcontroller (ATTiny85) and carry out a basic function test.



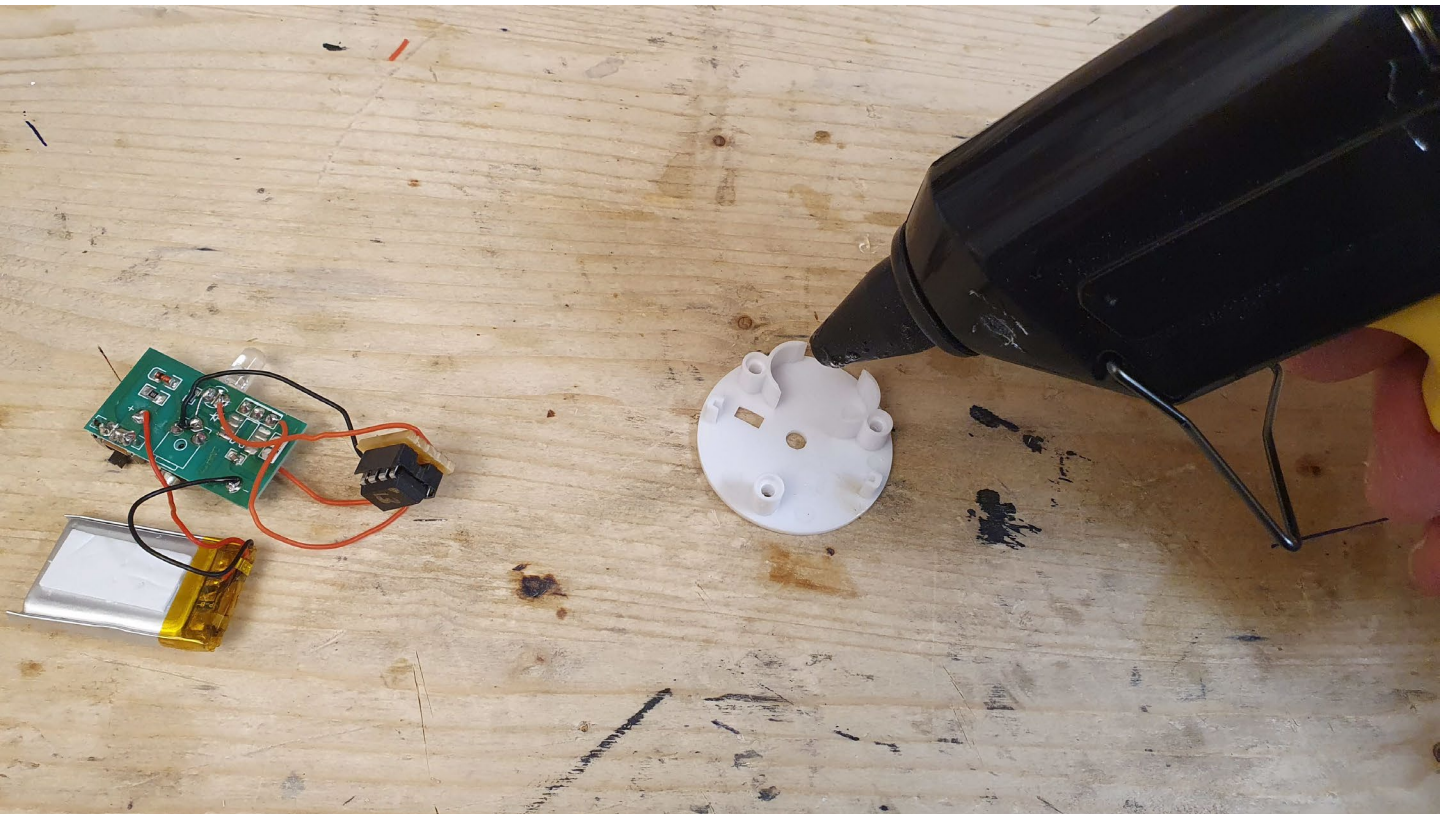Then we can glue the chip socket into place with some hot glue.



We put everything together and we're done!

